
CSE 311: Foundations of Computing

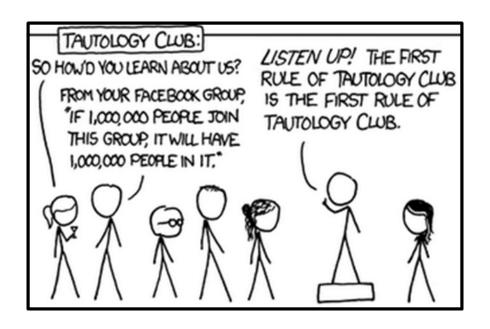Lecture 4: Boolean Algebra, Circuits, Canonical Forms



Last Time: Proofs of Equivalence

To show A is equivalent to B

 Apply a series of logical equivalences to sub-expressions to convert A to B

To show A is a tautology

 Apply a series of logical equivalences to sub-expressions to convert A to T

Logical Proofs

Identity

$$- p \wedge T \equiv p$$

$$- p \vee F \equiv p$$

Domination

$$- p \lor T \equiv T$$

$$-p \wedge F \equiv F$$

Idempotent

$$-\ p \vee p \equiv p$$

$$- p \wedge p \equiv p$$

Commutative

$$-\ p \vee q \equiv q \vee p$$

$$- p \wedge q \equiv q \wedge p$$

Associative

$$- (p \lor q) \lor r \equiv p \lor (q \lor r)$$
$$- (p \land q) \land r \equiv p \land (q \land r)$$

Distributive

$$- p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$$
$$- p \vee (q \wedge r) \equiv (p \vee q) \wedge (p \vee r)$$

Absorption

$$-\ p \lor (p \land q) \equiv p$$

$$- p \wedge (p \vee q) \equiv p$$

Negation

$$- p \lor \neg p \equiv T$$

$$-p \land \neg p \equiv F$$

De Morgan's Laws

$$\neg (p \land q) \equiv \neg p \lor \neg q$$
$$\neg (p \lor q) \equiv \neg p \land \neg q$$

Law of Implication

$$p \to q \equiv \neg p \vee q$$

Contrapositive

$$p \rightarrow q \equiv \neg q \rightarrow \neg p$$

Biconditional

$$p \leftrightarrow q \equiv (p \rightarrow q) \land (q \rightarrow p)$$

Double Negation

$$p \equiv \neg \neg p$$

Example:

Let A be " $\neg p \lor (p \lor p)$ ".

Our general proof looks like:

$$\neg p \lor (p \lor p) \equiv ($$
 $\equiv ($
 $\equiv \mathbf{T}$

Logical Proofs

Identity

$$- p \wedge T \equiv p$$

$$- p \vee F \equiv p$$

Domination

$$- p \lor T \equiv T$$

$$-p \wedge F \equiv F$$

Idempotent

$$-\ p \vee p \equiv p$$

$- p \wedge p \equiv p$

Commutative

$$- p \lor q \equiv q \lor p$$
$$- p \land q \equiv q \land p$$

Associative

$$- (p \lor q) \lor r \equiv p \lor (q \lor r)$$
$$- (p \land q) \land r \equiv p \land (q \land r)$$

Distributive

$$- p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$$
$$- p \vee (q \wedge r) \equiv (p \vee q) \wedge (p \vee r)$$

Absorption

$$- p \lor (p \land q) \equiv p$$
$$- p \land (p \lor q) \equiv p$$

Negation

$$- p \lor \neg p \equiv T$$
$$- p \land \neg p \equiv F$$

De Morgan's Laws

$$\neg (p \land q) \equiv \neg p \lor \neg q$$
$$\neg (p \lor q) \equiv \neg p \land \neg q$$

Law of Implication

$$p \to q \ \equiv \ \neg p \lor q$$

Contrapositive

$$p \to q \equiv \neg q \to \neg p$$

Biconditional

$$p \leftrightarrow q \equiv (p \rightarrow q) \land (q \rightarrow p)$$

Double Negation

$$p \equiv \neg \neg p$$

Example:

Let A be " $\neg p \lor (p \lor p)$ ".

Our general proof looks like:

$$\neg p \lor (p \lor p) \equiv (\neg p \lor p) \text{ Idempotent}$$

$$\equiv (p \lor \neg p) \text{ Commutative}$$

$$\equiv \mathbf{T} \text{ Negation}$$

Prove these propositions are equivalent

Prove: $p \land (p \rightarrow r) \equiv p \land r$

$$p \land (p \rightarrow r) \equiv$$

$$\equiv$$

$$\equiv$$

$$\equiv$$

$$\equiv p \land r$$

- Identity
 - $-\ p \wedge \mathbf{T} \equiv p$
 - $p \lor F \equiv p$
- Domination
 - $p \lor T \equiv T$
 - $-p \wedge F \equiv F$
- Idempotent
 - $-\ p \vee p \equiv p$
 - $p \wedge p \equiv p$
- Commutative
 - $p \lor q \equiv q \lor p$ $p \land q \equiv q \land p$

- Associative
 - $(p \lor q) \lor r \equiv p \lor (q \lor r)$
 - $-(p \wedge q) \wedge r \equiv p \wedge (q \wedge r)$
- Distributive
 - $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$
 - $p \lor (q \land r) \equiv (p \lor q) \land (p \lor r)$
- Absorption
 - $p \lor (p \land q) \equiv p$
 - $p \land (p \lor q) \equiv p$
- Negation
 - $p \lor \neg p \equiv T$
 - $-p \land \neg p \equiv F$

De Morgan's Laws

$$\neg (p \land q) \equiv \neg p \lor \neg q$$
$$\neg (p \lor q) \equiv \neg p \land \neg q$$

Law of Implication

$$p \rightarrow q \equiv \neg p \lor q$$

Contrapositive

$$p \to q \ \equiv \ \neg q \to \neg p$$

Biconditional

$$p \leftrightarrow q \, \equiv \, (p {\to} \, q) \wedge (q \to p)$$

Double Negation

$$p \equiv \neg \neg p$$

Prove these propositions are equivalent

Prove: $p \land (p \rightarrow r) \equiv p \land r$

$$p \land (p \rightarrow r) \equiv p \land (\neg p \lor r)$$
 $\equiv (p \land \neg p) \lor (p \land r)$ Dist $\equiv \mathbf{F} \lor (p \land r)$ Neg $\equiv (p \land r) \lor \mathbf{F}$ Com $\equiv p \land r$ Iden

Law of Implication

Distributive

Negation

Commutative

Identity

Identity

$$- p \wedge T \equiv p$$

$$- p \vee F \equiv p$$

Domination

$$- p \lor T \equiv T$$

$$-p \wedge F \equiv F$$

Idempotent

$$-\ p \vee p \equiv p$$

$$- p \wedge p \equiv p$$

Commutative

$$-\ p \lor q \equiv q \lor p$$

$$- p \wedge q \equiv q \wedge p$$

Associative

$$-\ (p\vee q)\vee r\equiv p\vee (q\vee r)$$

$$- (p \land q) \land r \equiv p \land (q \land r)$$

Distributive

$$- p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$$

$$- p \lor (q \land r) \equiv (p \lor q) \land (p \lor r)$$

Absorption

$$- p \lor (p \land q) \equiv p$$

$$- p \land (p \lor q) \equiv p$$

Negation

$$- p \lor \neg p \equiv T$$

$$-p \land \neg p \equiv F$$

De Morgan's Laws

$$\neg(p \land q) \equiv \neg p \lor \neg q$$
$$\neg(p \lor q) \equiv \neg p \land \neg q$$

Law of Implication

$$p \rightarrow q \equiv \neg p \lor q$$

Contrapositive

$$p \to q \ \equiv \ \neg q \to \neg p$$

Biconditional

$$p \leftrightarrow q \equiv (p {\rightarrow} \, q) \wedge (q \rightarrow p)$$

Double Negation

$$p \equiv \neg \neg p$$

Prove this is a Tautology: Option 1

$$(p \land r) \rightarrow (r \lor p)$$

Use a series of equivalences like so:

$$(p \land r) \rightarrow (r \lor p) \equiv$$

Identity

- $-p \wedge T \equiv p$
- $p \vee F \equiv p$

Domination

- $p \lor T \equiv T$
- $-p \wedge F \equiv F$

Idempotent

- $p \lor p \equiv p$
- $p \wedge p \equiv p$

Commutative

- $p \lor q \equiv q \lor p$
- $p \wedge q \equiv q \wedge p$

Associative

- $-(p \lor q) \lor r \equiv p \lor (q \lor r)$
- $-(p \wedge q) \wedge r \equiv p \wedge (q \wedge r)$

Distributive

- $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$
- $p \lor (q \land r) \equiv (p \lor q) \land (p \lor r)$

Absorption

- $p \lor (p \land q) \equiv p$
- $p \land (p \lor q) \equiv p$

Negation

- $p \lor \neg p \equiv T$
- $-p \land \neg p \equiv F$

Prove this is a Tautology: Option 1

$$(p \land r) \rightarrow (r \lor p)$$

Use a series of equivalences like so:

$$(p \land r) \rightarrow (r \lor p) \equiv \neg (p \land r) \lor (r \lor p)$$

$$\equiv (\neg p \lor \neg r) \lor (r \lor p)$$

$$\equiv \neg p \lor (\neg r \lor (r \lor p))$$

$$\equiv \neg p \lor ((\neg r \lor r) \lor p)$$

$$= \neg p \lor ((\neg r \lor r) \lor p)$$

$$= \neg p \lor (p \lor (\neg r \lor r))$$

$$\equiv \neg p \lor (p \lor (\neg r \lor r))$$

$$\equiv (\neg p \lor p) \lor (\neg r \lor r)$$

$$= (p \lor \neg p) \lor (r \lor \neg r)$$

 $\equiv \mathsf{T} \vee \mathsf{T}$

Associative

- $-(p \lor q) \lor r \equiv p \lor (q \lor r)$
- $-(p \wedge q) \wedge r \equiv p \wedge (q \wedge r)$

Distributive

- $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$
- $p \lor (q \land r) \equiv (p \lor q) \land (p \lor r)$

Absorption

- $p \lor (p \land q) \equiv p$
- $p \land (p \lor q) \equiv p$

Negation

- $p \lor \neg p \equiv T$
- $-p \land \neg p \equiv F$

Law of Implication

De Morgan

Associative

Associative

Commutative

Associative

Commutative (twice)

Negation (twice)

Domination/Identity

Domination

- $p \lor T \equiv T$
- $-p \wedge F \equiv F$

Idempotent

- $p \lor p \equiv p$
- $-p \wedge p \equiv p$

Commutative

- $p \lor q \equiv q \lor p$
- $p \wedge q \equiv q \wedge p$

Prove this is a Tautology: Option 2

$$(p \land r) \rightarrow (r \lor p)$$

Make a Truth Table and show:

$$(p \land r) \rightarrow (r \lor p) \equiv \mathbf{T}$$

p	r	$p \wedge r$	$r \lor p$	$(p \land r) \rightarrow (r \lor p)$
Т	Т	Т	Т	Т
Т	F	F	Т	Т
F	Т	F	Т	Т
F	F	F	F	Т

Boolean Logic

Combinational Logic

- output = F(input)


Sequential Logic

- $-\operatorname{output}_t = \operatorname{F}(\operatorname{output}_{t-1}, \operatorname{input}_t)$
 - output dependent on history
 - concept of a time step (clock, t)

Boolean Logic

Combinational Logic

- output = F(input)

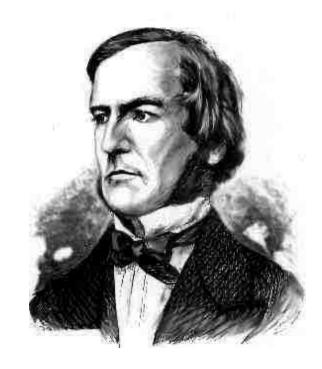


Boolean Algebra: another notation for logic consisting of...

- a set of elements B = $\{0, 1\}$
- binary operations { + , } (OR, AND)
- and a unary operation { ' } (NOT)

Boolean Algebra

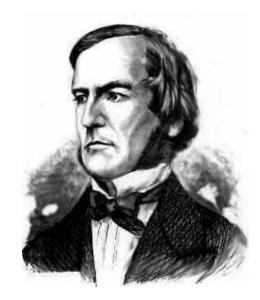- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing {0, 1}
 - binary operations { + , }
 - and a unary operation { ' }
 - such that the following axioms hold:



```
For any a, b, c in B:
1. closure:
                                       a + b is in B
                                                                                     a • b is in B
2. commutativity:
                                      a + b = b + a
                                                                                     a \cdot b = b \cdot a
                                 a + (b + c) = (a + b) + c a \cdot (b \cdot c) = (a \cdot b) \cdot c

a + (b \cdot c) = (a + b) \cdot (a + c) a \cdot (b + c) = (a \cdot b) + (a \cdot c)
3. associativity:
                                                                                     a \cdot (b + c) = (a \cdot b) + (a \cdot c)
4. distributivity:
                                      a + 0 = a
                                                                                     a \cdot 1 = a
5. identity:
6. complementarity:
                                      a + a' = 1
                                                                                     a \cdot a' = 0
                                      a + 1 = 1
                                                                                     a \cdot 0 = 0
7. null:
8. idempotency:
                                      a + a = a
                                                                                     a \cdot a = a
9. involution:
                                      (a')' = a
```

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining at the start of a given day of the week.

- Inputs: Day of the Week, Lecture/Section flag
- Output: Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: 2

Input: (Monday, Section) Output: 1


Implementation in Software

```
public int classesLeftInMorning(int weekday, boolean isLecture) {
    switch (weekday) {
        case SUNDAY:
        case MONDAY:
            return isLecture ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return isLecture ? 2 : 1;
        case THURSDAY:
            return isLecture ? 1 : 1;
        case FRIDAY:
            return isLecture ? 1 : 0;
        case SATURDAY:
            return isLecture ? 0 : 0;
```

Implementation with Combinational Logic

Encoding:

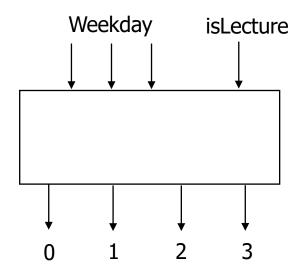- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



Defining Our Inputs!

Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	(000) ₂
Monday	1	(001) ₂
Tuesday	2	(010) ₂
Wednesday	3	(011) ₂
Thursday	4	(100) ₂
Friday	5	(101) ₂
Saturday	6	(110) ₂

Converting to a Truth Table!

```
case SUNDAY or MONDAY:
    return isLecture ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return isLecture ? 2 : 1;
case THURSDAY:
    return isLecture ? 1 : 1;
case FRIDAY:
    return isLecture ? 1 : 0;
case SATURDAY:
    return isLecture ? 0 : 0;
```

Wee	kday	isLecture	c _o	$\mathbf{c_1}$	c ₂	C ₃
SUN	000	0				
SUN	000	1				
MON	001	0				
MON	001	1				
TUE	010	0				
TUE	010	1				
WED	011	0				
WED	011	1				
THU	100	-				
FRI	101	0				
FRI	101	1				
SAT	110	-				
-	111	-				

Converting to a Truth Table!

```
case SUNDAY or MONDAY:
    return isLecture ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return isLecture ? 2 : 1;
case THURSDAY:
    return isLecture ? 1 : 1;
case FRIDAY:
    return isLecture ? 1 : 0;
case SATURDAY:
    return isLecture ? 0 : 0;
```

Wee	kday	isLecture	c _o	$\mathbf{c_1}$	c ₂	C ₃
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

	$d_2d_1d_0$	L	c ₀	$\mathbf{c_1}$	c ₂	c ₃
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Let's begin by finding an expression for c_3 . To do this, we look at the rows where $c_3 = 1$ (true).

	$d_2d_1d_0$	L	c ₀	c ₁	c ₂	C ₃
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

	$d_2d_1d_0$	L	c ₀	c ₁	C ₂	C ₃
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

	$d_2d_1d_0$	L	c ₀	c ₁	c ₂	C ₃	
SUN	000	0	0	1	0	0	
SUN	000	1	0	0	0	1	d ₂ == 0 && d ₁ == 0 && d ₀ == 0 && L
MON	001	0	0	1	0	0	
MON	001	1	0	0	0	1	d ₂ == 0 && d ₁ == 0 && d ₀ == 1 && L
TUE	010	0	0	1	0	0	Splitting up the bits of the
TUE	010	1	0	0	1	0	so, we can write a formul
WED	011	0	0	1	0	0	,
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	
	MON MON TUE TUE WED THU FRI FRI SAT	SUN 000 SUN 000 MON 001 TUE 010 TUE 010 WED 011 THU 100 FRI 101 FRI 101 SAT 110	SUN 000 0 SUN 000 1 MON 001 0 MON 001 1 TUE 010 0 TUE 010 1 WED 011 0 WED 011 1 THU 100 - FRI 101 0 FRI 101 1 SAT 110 -	SUN 000 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0	SUN 000 0 0 1 SUN 000 1 0 0 MON 001 0 0 1 MON 001 1 0 0 TUE 010 0 0 1 TUE 010 1 0 0 WED 011 0 0 1 WED 011 1 0 0 THU 100 - 0 1 FRI 101 0 1 0 FRI 101 1 0 1 SAT 110 - 1 0	SUN 000 0 0 1 0 SUN 000 1 0 0 0 MON 001 0 0 1 0 MON 001 1 0 0 0 TUE 010 0 1 0 TUE 010 1 0 0 1 WED 011 1 0 0 1 THU 100 - 0 1 0 FRI 101 0 1 0 0 SAT 110 - 1 0 0	SUN 000 0 0 1 0 0 1 0 0 1 0 0 0 0 1 0 0 0 0 1 0

	$d_2d_1d_0$	L	c ₀	c ₁	c ₂	c ₃
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

	$d_2d_1d_0$	L	c ₀	c ₁	c ₂	C ₃
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

How do we combine them?

	$d_2d_1d_0$	L	c ₀	c ₁	C ₂	C ₃
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

	$d_2d_1d_0$	L	c ₀	c ₁	C ₂	C ₃	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
SUN	000	0	0	1	0	0	Now, we do c ₂ .
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

			1)		
	$d_2d_1d_0$	L	c _o	C ₁	C ₂	C ₃	Now, we do c₁:
SUN	000	0	0	1	0	0	
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	-
-	111	-	1	0	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$ $c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$

	$d_2d_1d_0$	L	c ₀	C ₁	C ₂	C ₃	Now, we do c₁:
SUN	000	0	0	1	0	0	d ₂ '•d ₁ '•d ₀ '•L'
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	d ₂ ' • d ₁ ' • d ₀ • L'
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	d ₂ ' • d ₁ • d ₀ ' • L'
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	d ₂ ' • d ₁ • d ₀ • L'
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	???
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	d ₂ • d ₁ ' • d ₀ • L
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1'$
							$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1$


	$d_2d_1d_0$	L	c ₀	C ₁	C ₂	C ₃	Now, we do c₁ :
SUN	000	0	0	1	0	0	d ₂ ' • d ₁ ' • d ₀ ' • L'
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	d ₂ ' • d ₁ ' • d ₀ • L'
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	No matter what L is
THU	100	-	0	1	0	0	d ₂ •d ₁ '•d ₀ ' we always say it's 1 So, we don't need L
FRI	101	0	1	0	0	0	in the expression.
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$ $c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$

	$d_2d_1d_0$	L	c ₀	C ₁	C ₂	C ₃	Now, we do c₁ :
SUN	000	0	0	1	0	0	d ₂ '•d ₁ '•d ₀ '•L'
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	No matter what L i
THU	100	-	0	1	0	0	d₂ • d₁' • d₀' we always say it's : So, we don't need
FRI	101	0	1	0	0	0	in the expression
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
-	111	-	1	0	0	0	$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$

	$d_2d_1d_0$	L	c ₀	c ₁	C ₂	C ₃	$\mathbf{c_1} = \mathbf{d_2'} \cdot \mathbf{d_1'} \cdot \mathbf{d_0'} \cdot \mathbf{L'} + \mathbf{d_2'} \cdot \mathbf{d_1'} \cdot \mathbf{d_0}$
SUN	000	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$
SUN	000	1	0	0	0	1	$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1$
MON	001	0	0	1	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	Finally, we do c ₀ :
FRI	101	0	1	0	0	0	d ₂ • d ₁ ' • d ₀ • L'
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	d ₂ • d ₁ • d ₀ '
-	111	-	1	0	0	0	$d_2 \cdot d_1 \cdot d_0$


$$\begin{aligned} c_0 &= d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0 \\ c_1 &= d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L \\ c_2 &= d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L \\ c_3 &= d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L \end{aligned}$$

Here's c₃ as a circuit:

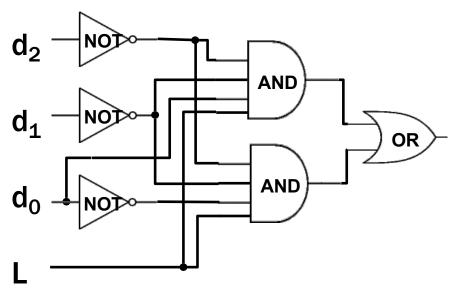

Boolean Algebra

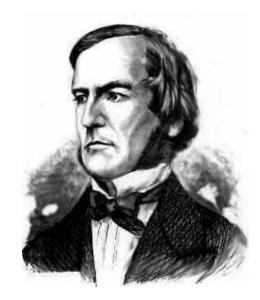- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing {0, 1}
 - binary operations { + , }
 - and a unary operation { ' }
 - such that the following axioms hold:



```
For any a, b, c in B:
1. closure:
                                       a + b is in B
                                                                                     a • b is in B
2. commutativity:
                                      a + b = b + a
                                                                                     a \cdot b = b \cdot a
                                 a + (b + c) = (a + b) + c a \cdot (b \cdot c) = (a \cdot b) \cdot c

a + (b \cdot c) = (a + b) \cdot (a + c) a \cdot (b + c) = (a \cdot b) + (a \cdot c)
3. associativity:
                                                                                     a \cdot (b + c) = (a \cdot b) + (a \cdot c)
4. distributivity:
                                      a + 0 = a
                                                                                     a \cdot 1 = a
5. identity:
6. complementarity:
                                      a + a' = 1
                                                                                     a \cdot a' = 0
                                      a + 1 = 1
                                                                                     a \cdot 0 = 0
7. null:
8. idempotency:
                                      a + a = a
                                                                                     a \cdot a = a
9. involution:
                                      (a')' = a
```

Simplification using Boolean Algebra

uniting:

10.
$$a \cdot b + a \cdot b' = a$$

absorption:

11.
$$a + a \cdot b = a$$

12.
$$(a + b') \cdot b = a \cdot b$$

factoring:

13.
$$(a + b) \cdot (a' + c) =$$

 $a \cdot c + a' \cdot b$

consensus:

14.
$$(a \cdot b) + (b \cdot c) + (a' \cdot c) = a \cdot b + a' \cdot c$$

de Morgan's:

15.
$$(a + b + ...)' = a' \cdot b' \cdot ...$$

10D.
$$(a + b) \cdot (a + b') = a$$

11D.
$$a \cdot (a + b) = a$$

12D.
$$(a \cdot b') + b = a + b$$

13D.
$$a \cdot b + a' \cdot c =$$

(a + c) \cdot (a' + b)

14D.
$$(a + b) \cdot (b + c) \cdot (a' + c) = (a + b) \cdot (a' + c)$$

15D.
$$(a \cdot b \cdot ...)' = a' + b' + ...$$

Simplifying using Boolean Algebra

```
c3 = d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L
    = d2' \cdot d1' \cdot (d0' + d0) \cdot L
    = d2' • d1' • 1 • L
    = d2' • d1' • L
                                                       AND
               d1
                           NOT
```