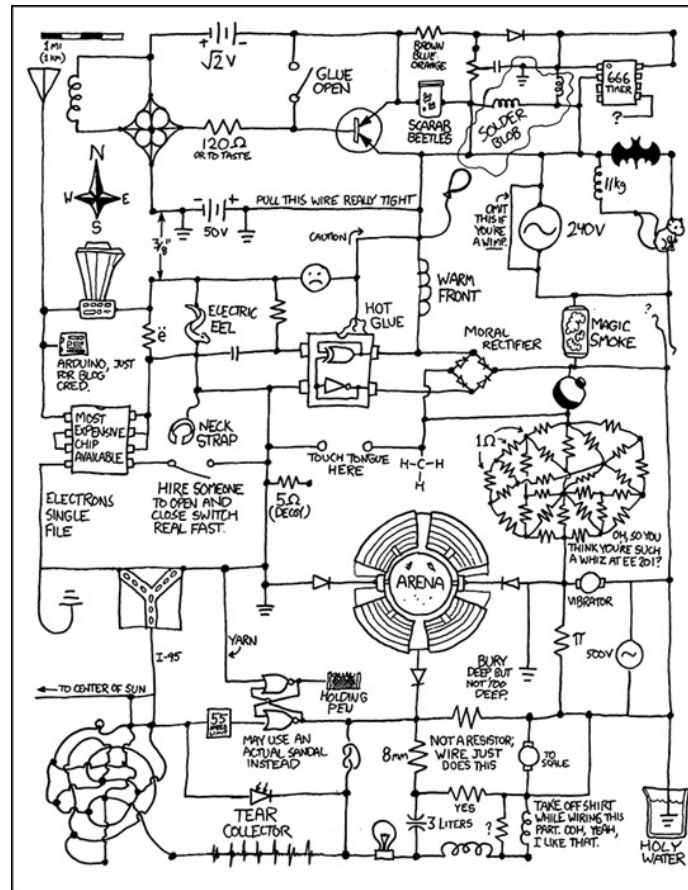


# CSE 311: Foundations of Computing

## Lecture 5: DNF, CNF and Predicate Logic



## Warm-up Exercise

---

- Create a Boolean Algebra expression for  $C$  below in terms of the variables  $a$  and  $b$

$a$	$b$	$C(a, b)$
1	1	0
1	0	1
0	1	1
0	0	0

$$ab' + a'b$$

## Warm-up Exercise

---

- Create a Boolean Algebra expression for “ $c$ ” below in terms of the variables  $a$  and  $b$

$$c = ab' + a'b$$

- Draw this as a circuit (using AND, OR, NOT)

# Combinational Logic Example

---

case SUNDAY or MONDAY:

    return isLecture ? 3 : 1;

case TUESDAY or WEDNESDAY:

    return isLecture ? 2 : 1;

case THURSDAY:

    return isLecture ? 1 : 1;

case FRIDAY:

    return isLecture ? 1 : 0;

case SATURDAY:

    return isLecture ? 0 : 0;

Weekday		isLecture	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

# Truth Table to Logic (Part 3)

	$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Now, we do  $c_1$ :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

	$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	???
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

	$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

No matter what L is,  
we always say it's 1.  
So, we don't need L  
in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 4)

---


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Here's  $c_3$  as a circuit:

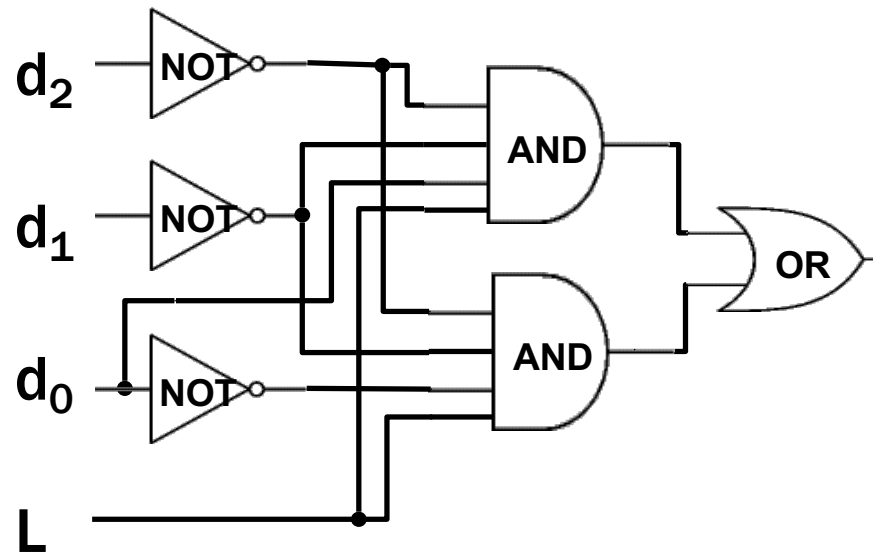



# Important Corollaries of this Construction


---

- $\neg, \wedge, \vee$  can implement any Boolean function  
we didn't need any others to do this
- **Actually, just  $\neg, \wedge$  (or  $\neg, \vee$ ) are enough**  
follows by De Morgan's laws
- **Actually, just NAND (or NOR)**
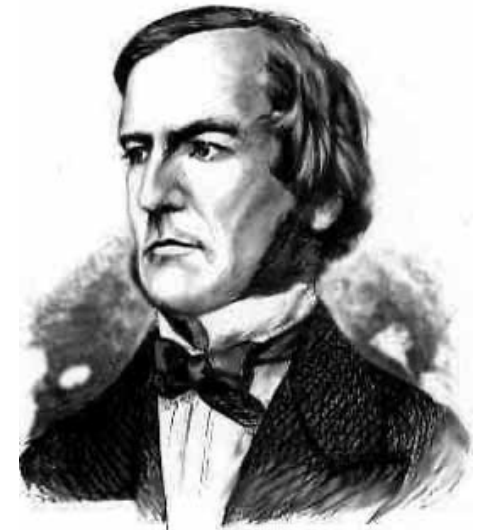
# Boolean Algebra

---

- Usual notation used in circuit design
- Boolean algebra
  - a set of elements  $B$  containing  $\{0, 1\}$
  - binary operations  $\{ + , \cdot \}$
  - and a unary operation  $\{ ' \}$
  - such that the following axioms hold:



For any  $a, b, c$  in  $B$ :

- |                     |   |
|---------------------|---|
| 1. closure:         | $a + b$ is in $B$                         |
| 2. commutativity:   | $a + b = b + a$                           |
| 3. associativity:   | $a + (b + c) = (a + b) + c$               |
| 4. distributivity:  | $a + (b \cdot c) = (a + b) \cdot (a + c)$ |
| 5. identity:        | $a + 0 = a$                               |
| 6. complementarity: | $a + a' = 1$                              |
| 7. null:            | $a + 1 = 1$                               |
| 8. idempotency:     | $a + a = a$                               |
| 9. involution:      | $(a')' = a$                               |

- |   |
|---|
| $a \cdot b$ is in $B$                         |
| $a \cdot b = b \cdot a$                       |
| $a \cdot (b \cdot c) = (a \cdot b) \cdot c$   |
| $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ |
| $a \cdot 1 = a$                               |
| $a \cdot a' = 0$                              |
| $a \cdot 0 = 0$                               |
| $a \cdot a = a$                               |

# Simplification using Boolean Algebra

---

## uniting:

$$10. a \cdot b + a \cdot b' = a$$

$$10D. (a + b) \cdot (a + b') = a$$

## absorption:

$$11. a + a \cdot b = a$$

$$11D. a \cdot (a + b) = a$$

$$12. (a + b') \cdot b = a \cdot b$$

$$12D. (a \cdot b') + b = a + b$$

## factoring:

$$13. (a + b) \cdot (a' + c) = \\ a \cdot c + a' \cdot b$$

$$13D. a \cdot b + a' \cdot c = \\ (a + c) \cdot (a' + b)$$

## consensus:

$$14. (a \cdot b) + (b \cdot c) + (a' \cdot c) = \\ a \cdot b + a' \cdot c$$

$$14D. (a + b) \cdot (b + c) \cdot (a' + c) = \\ (a + b) \cdot (a' + c)$$

## de Morgan's:


$$15. (a + b + \dots)' = a' \cdot b' \cdot \dots$$

$$15D. (a \cdot b \cdot \dots)' = a' + b' + \dots$$
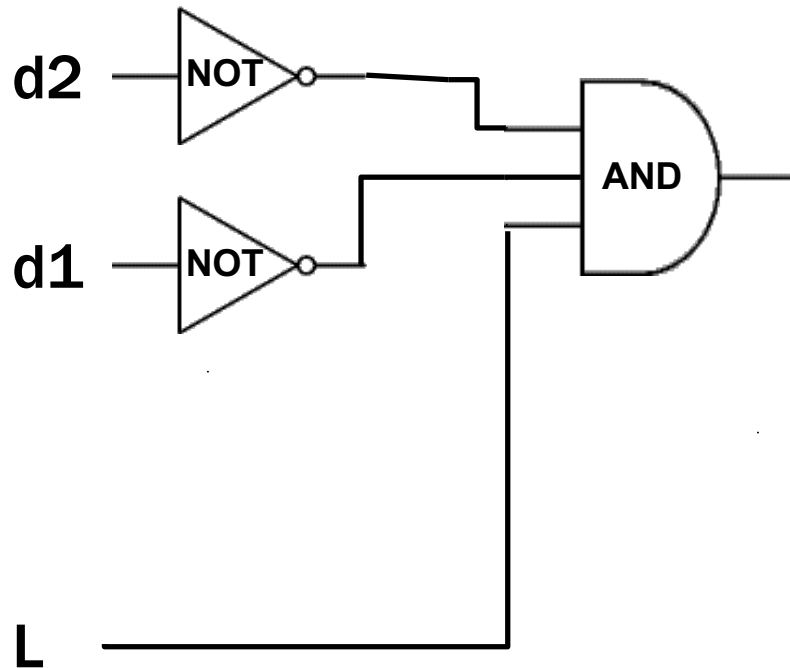
# Simplifying using Boolean Algebra

---

$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\&= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\&= d2' \cdot d1' \cdot 1 \cdot L \\&= d2' \cdot d1' \cdot L\end{aligned}$$



# 1-bit Binary Adder

---

A	$0 + 0 = 0$ (with $C_{OUT} = 0$ )
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$ )
S	$1 + 0 = 1$ (with $C_{OUT} = 0$ )
( $C_{OUT}$ )	$1 + 1 = 0$ (with $C_{OUT} = 1$ )

# 1-bit Binary Adder

---

A	$0 + 0 = 0$ (with $C_{OUT} = 0$ )
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$ )
S	$1 + 0 = 1$ (with $C_{OUT} = 0$ )
( $C_{OUT}$ )	$1 + 1 = 0$ (with $C_{OUT} = 1$ )

**Idea: chain these together to add larger numbers**

Recall from  
elementary school:


$$\begin{array}{r} 248 \\ + 375 \\ \hline \end{array}$$

# 1-bit Binary Adder

A	$0 + 0 = 0$ (with $C_{OUT} = 0$ )
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$ )
S	$1 + 0 = 1$ (with $C_{OUT} = 0$ )
( $C_{OUT}$ )	$1 + 1 = 0$ (with $C_{OUT} = 1$ )

**Idea:** These are chained together with a carry-in

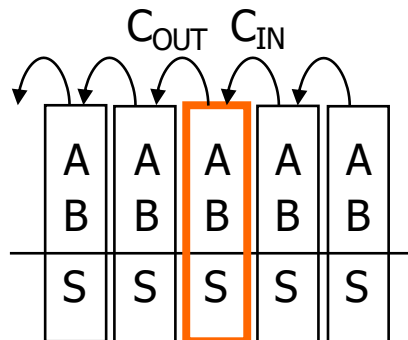( $C_{IN}$ )  
A  
+ B  
S  
( $C_{OUT}$ )




	1	1	0	0	
$C_{OUT}$	0	1	1	1	0
$C_{IN}$	0	1	1	0	1
S	1	1	0	1	1

# 1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out


A	B	C <sub>IN</sub>	C <sub>OUT</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

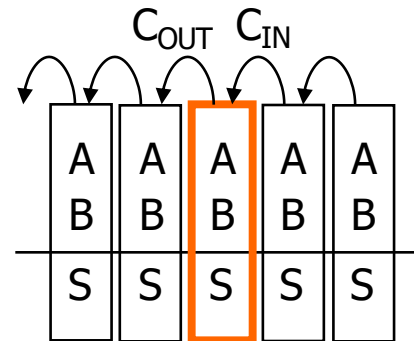


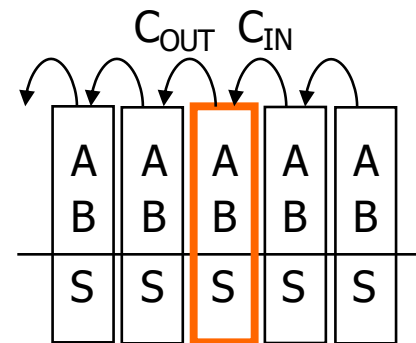
# 1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C <sub>IN</sub>	C <sub>OUT</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for S

$$A' \cdot B' \cdot C_{IN}$$

$$A' \cdot B \cdot C_{IN}'$$


$$A \cdot B' \cdot C_{IN}'$$

$$A \cdot B \cdot C_{IN}$$

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$
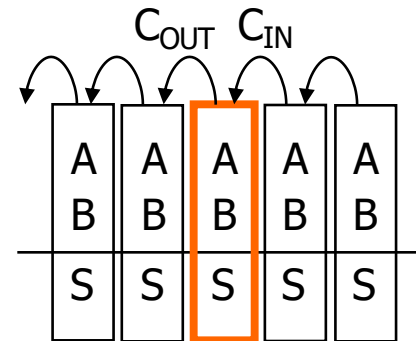
# 1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C <sub>IN</sub>	C <sub>OUT</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for C<sub>OUT</sub>

$$A' \cdot B \cdot C_{IN}$$

$$A \cdot B' \cdot C_{IN}$$

$$A \cdot B \cdot C_{IN}'$$


$$A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$
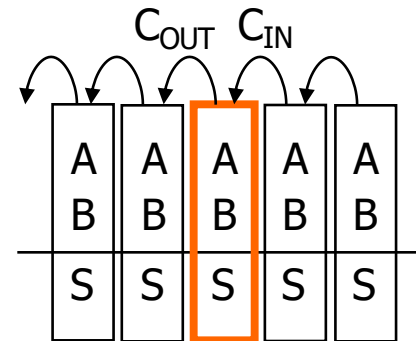
# 1-bit Binary Adder

- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C <sub>IN</sub>	C <sub>OUT</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

# Apply Theorems to Simplify Expressions

---

The theorems of Boolean algebra can simplify expressions

– e.g., full adder's carry-out function

$$\begin{aligned}\text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} + A B \text{Cin} \\ &= A' B \text{Cin} + A B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (A' + A) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (1) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} + A B \text{Cin} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (B' + B) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (1) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A \text{Cin} + A B (\text{Cin}' + \text{Cin}) \\ &= B \text{Cin} + A \text{Cin} + A B (1) \\ &= B \text{Cin} + A \text{Cin} + A B\end{aligned}$$

# Apply Theorems to Simplify Expressions

---


The theorems of Boolean algebra can simplify expressions

– e.g., full adder's carry-out function

$$\begin{aligned}\text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\ &= A' B \text{Cin} + A B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (A' + A) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (1) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (B' + B) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (1) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A \text{Cin} + A B (\text{Cin}' + \text{Cin}) \\ &= B \text{Cin} + A \text{Cin} + A B (1) \\ &= B \text{Cin} + A \text{Cin} + A B\end{aligned}$$

adding extra terms  
creates new factoring  
opportunities

# A 2-bit Ripple-Carry Adder

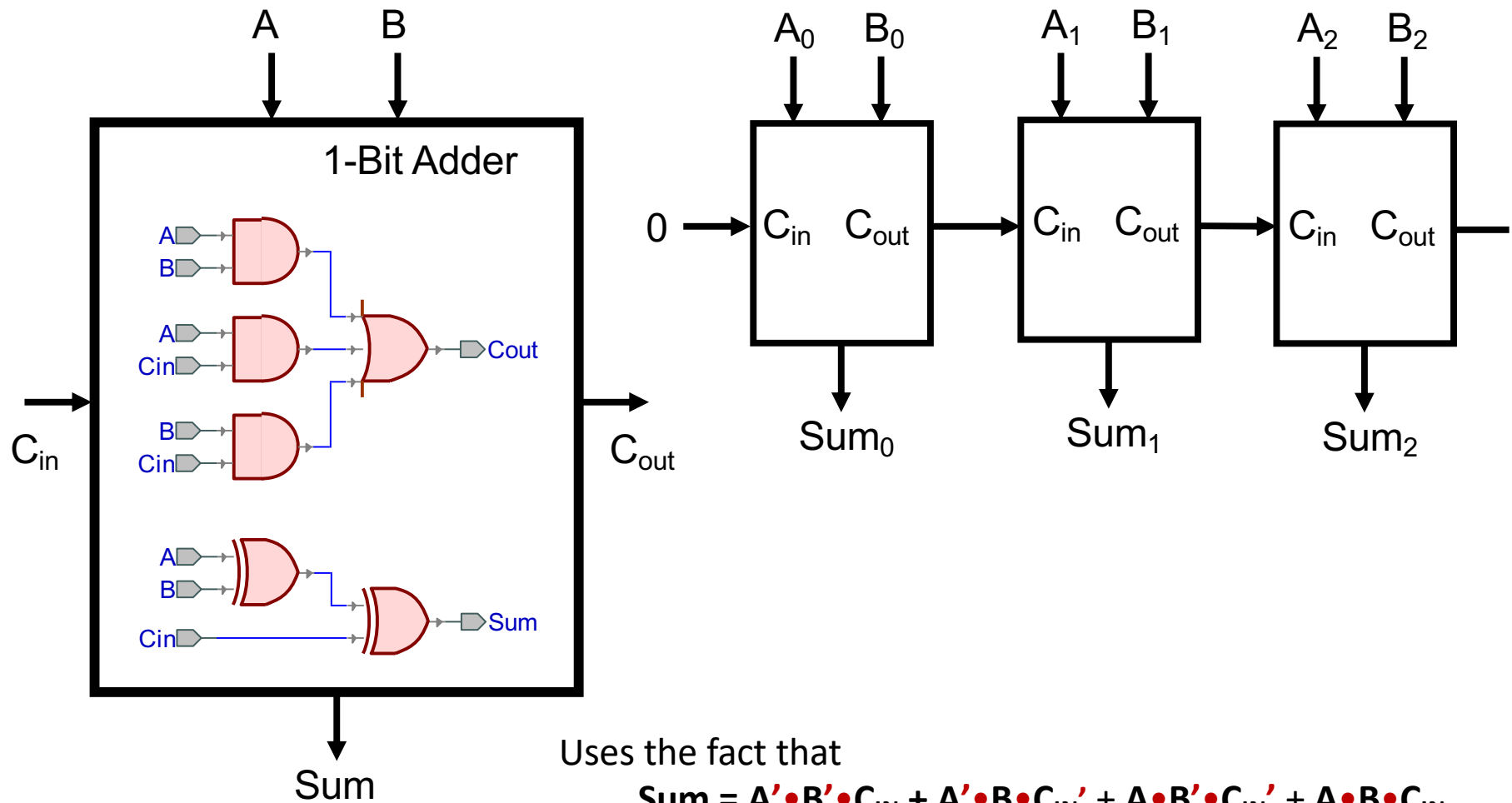

Uses the fact that

$$\text{Sum} = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

is equivalent to  $\text{Sum} = (A \oplus B) \oplus C_{IN}$

# Mapping Truth Tables to Logic Gates

Given a truth table:


1. Write the output in a table
2. Write the Boolean expression
3. Minimize the Boolean expression
4. Draw as gates
5. Map to available gates

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


③

$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$

④

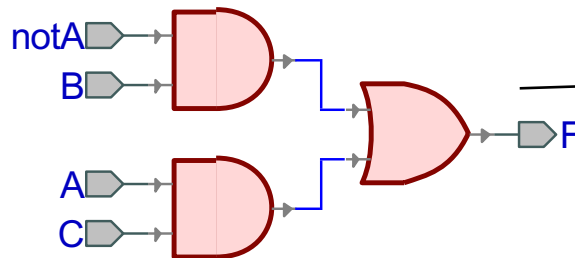

⑤

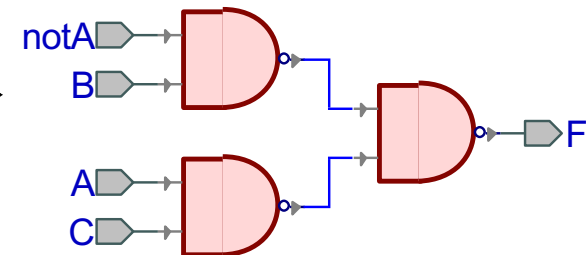

# Canonical Forms

---

- **Truth table is the unique signature of a 0/1 function**
- **The same truth table can have many gate realizations**
  - We've seen this already
  - Depends on how good we are at Boolean simplification
- **Canonical forms**
  - Standard forms for a Boolean expression
  - We all produce the same expression




# Sum-of-Products Canonical Form

- AKA **Disjunctive Normal Form (DNF)**
- AKA **Minterm Expansion**

③

Add the minterms together

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

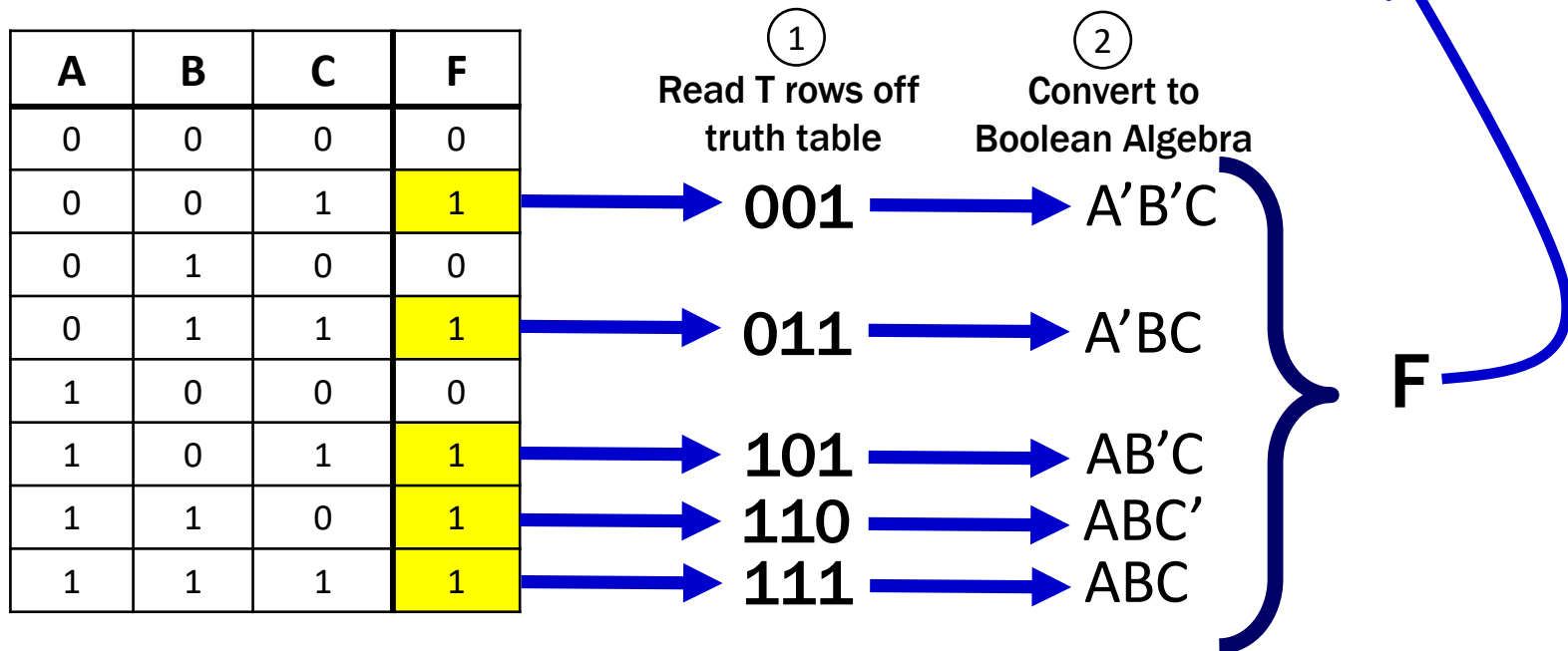

# Sum-of-Products Canonical Form

---

## Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	$ABC'$
1	1	1	$ABC$

**F in canonical form:**


$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

**canonical form  $\neq$  minimal form**

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$

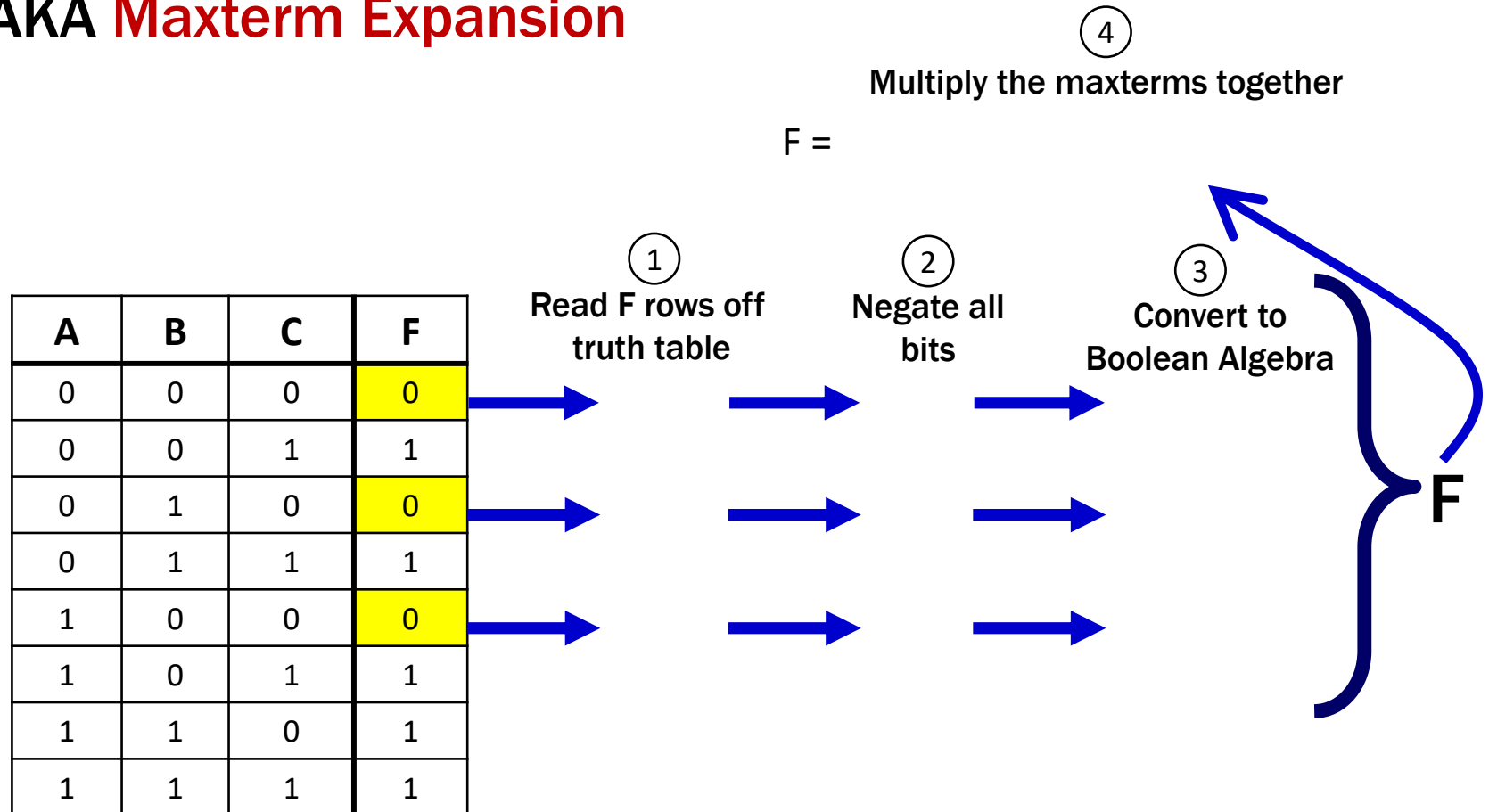
# Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**


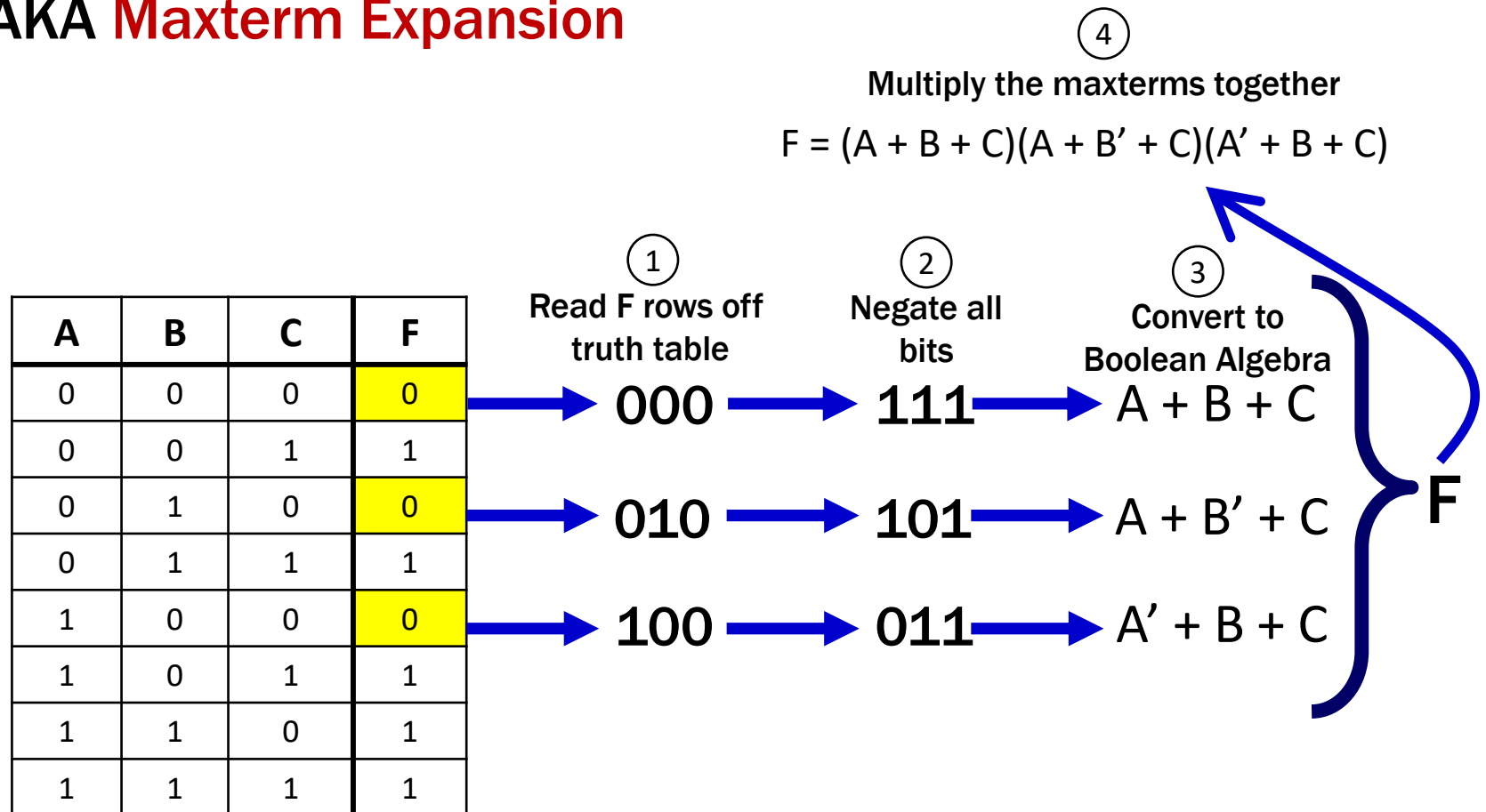
# Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**




# Product-of-Sums: Why does this procedure work?

---

## Useful Facts:

- We know  $(F')' = F$
- We know how to get a **minterm** expansion for  $F'$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

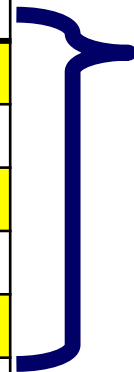
$$F' = A'B'C' + A'BC' + AB'C'$$

# Product-of-Sums: Why does this procedure work?

---

## Useful Facts:

- We know  $(F')' = F$
- We know how to get a **minterm** expansion for  $F'$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$F' = A'B'C' + A'BC' + AB'C'$$

Taking the complement of both sides...

$$(F')' = (A'B'C' + A'BC' + AB'C')'$$

And using DeMorgan/Comp....

$$F = (A'B'C')' (A'BC')' (AB'C')'$$

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

# Product-of-Sums Canonical Form

---

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	$A+B+C$
0	0	1	$A+B+C'$
0	1	0	$A+B'+C$
0	1	1	$A+B'+C'$
1	0	0	$A'+B+C$
1	0	1	$A'+B+C'$
1	1	0	$A'+B'+C$
1	1	1	$A'+B'+C'$

**F in canonical form:**

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

**canonical form  $\neq$  minimal form**

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$